

Template Week 2 – Logic

Student number:582310

Assignment 2.1: Parking lot

Which gates do you need?

Voor de parkeerplaats met drie sensoren heb je een AND-poort nodig. Het bord mag alleen “FULL” tonen wanneer alle drie de parkeerplekken bezet zijn; in logische termen betekent dat dat de output 1 wordt als en slechts als $P1=1$, $P2=1$ en $P3=1$. De AND-poort modelleert precies dit “alle voorwaarden moeten waar zijn”-gedrag: één vrije plek (een 0) is al genoeg om de output 0 te houden, dus pas bij drie bezette plekken (1,1,1) gaat de LED-strip aan.

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Assignment 2.2: Android or iPhone

Which gates do you need?

Voor de telefoonkiezen-situatie heb je een XOR-poort (Exclusive OR) nodig. De medewerker mag precies één telefoon kiezen: óf Android óf iPhone, maar niet beide en ook niet geen van beide. De XOR-poort geeft output 1 wanneer precies één van de twee inputs 1 is, en 0 wanneer ze beide 0 zijn of beide 1. Daarmee leg je het “één van de twee, niet beide” principe exact vast in de logica.

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
0	1	1
1	0	1
1	1	0

Assignment 2.3: Four NAND gates

Complete this table

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0


How can the design be simplified?

De schakeling met vier NAND-poorten doet exact hetzelfde als één enkele NAND-poort. Uit de truth table blijkt dat Q alleen 0 is wanneer A en B beide 1 zijn, en anders altijd 1. Het ontwerp kan dus eenvoudig worden vervangen door één NAND-poort, wat het circuit compacter en efficiënter maakt

Assignment 2.4: Getting to know Logisim evolution

Screenshot of the design with your name and student number in it:


Lucas Aversch
582310

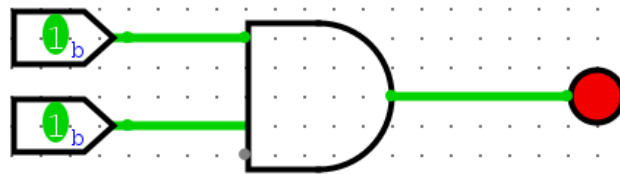

Assignment 2.5: SR Latch


Screenshot SR Latch in Logisim with your name and student number:

Lucas Aversch
582310

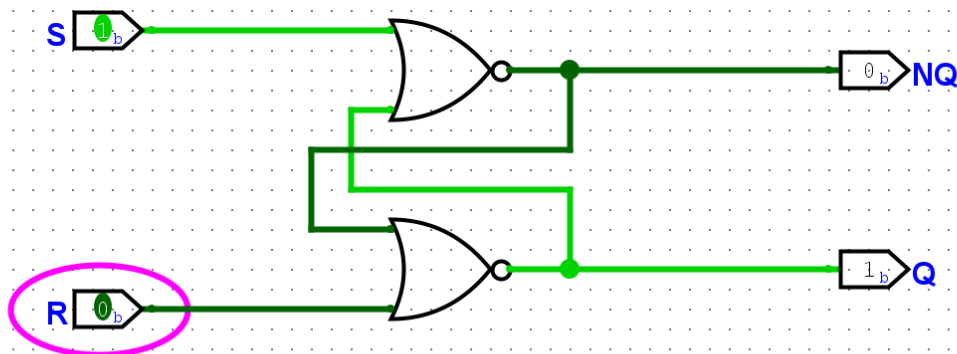

Assignment 2.6: Vending Machine

Screenshot Vending Machine in Logisim with your name and student number:

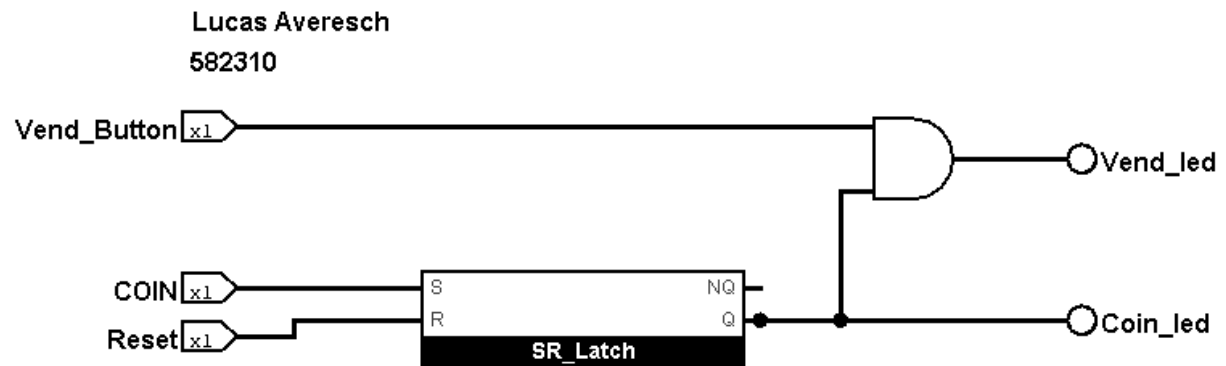

Assignment 2.7: Bitwise operators

1 — Even or odd (bitwise &)

```
public class Main {
    public static void main(String[] args) {
        int number = 5;

        if ((number & 1) == 1)
            System.out.println("number is odd");
        else
            System.out.println("number is even");
    }
}
```

#2 — Power of 2 (bitwise &)

```
public class Main {  
    public static void main(String[] args) {  
        int number = 4;  
  
        if (number > 0 && (number & (number - 1)) == 0)  
            System.out.println("number is a power of 2");  
        else  
            System.out.println("number isn't a power of 2");  
    }  
}
```

#3 — Check permissions (bitwise &)

```
public class Main {  
    public static void main(String[] args) {  
        final int READ = 4;  
        final int WRITE = 2;  
        final int EXECUTE = 1;  
  
        int userPermissions = 7; // rwx  
  
        if ((userPermissions & READ) == READ)  
            System.out.println("User has read permissions");  
        else  
            System.out.println("User can't read. No permissions.");  
    }  
}
```

#4 — Assign permissions (bitwise |)

```
public class Main {  
    public static void main(String[] args) {  
        final int READ = 4;  
        final int WRITE = 2;  
        final int EXECUTE = 1;  
  
        int userPermissions = 0;  
  
        userPermissions = userPermissions | READ | EXECUTE;  
  
        System.out.println("User permissions: " + userPermissions);  
    }  
}
```

#5 — Update permissions (bitwise ^)

```
public class Main {  
    public static void main(String[] args) {  
        final int READ = 4;  
        final int WRITE = 2;  
        final int EXECUTE = 1;  
  
        int userPermissions = 6; // READ + WRITE  
  
        userPermissions = userPermissions ^ WRITE;  
  
        System.out.println("User permissions: " + userPermissions);  
    }  
}
```

#6 — Two's complement (bitwise ~)

```
public class Main {  
    public static void main(String[] args) {  
        int number = 5;  
  
        number = ~number + 1;  
  
        System.out.println("Number: " + number);  
    }  
}
```

#7 — Display binary, octal, hex

```
public class Main {  
    public static void main(String[] args) {  
  
        int number = 10;  
  
        System.out.println("Decimal integer: " + number);  
  
        String binary = Integer.toBinaryString(number);  
        String octal = Integer.toOctalString(number);  
        String hexadecimal = Integer.toHexString(number);  
  
        System.out.println("Binary representation: " + binary);  
        System.out.println("Octal representation: " + octal);  
        System.out.println("Hexadecimal representation: " + hexadecimal);  
    }  
}
```

Assignment 2.8: Java Application Bit Calculations

Create a java program that accepts user input and presents a menu with options.

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Keep this application because you need to expand it in week 6 for calculating network segments.

Paste source code here, with a screenshot of a working application.

```
import java.util.Scanner;
```

```
public class BitCalculator {
```

```
    public static void main(String[] args) {
```

```
        Scanner input = new Scanner(System.in);
```

```
        while (true) {
```

```
            System.out.println("=== Bitwise Calculator ===");
```

```
            System.out.println("1. Is number odd?");
```

```
            System.out.println("2. Is number a power of 2?");
```

```
            System.out.println("3. Two's complement of number");
```

```
            System.out.println("4. Exit");
```

```
            System.out.print("Choose an option: ");
```

```
            int choice = input.nextInt();
```

```
            if (choice == 4) {
```

```
                System.out.println("Exiting...");
```

```
                break;
```

```
            }
```



```

System.out.print("Enter a number: ");

int number = input.nextInt();

switch (choice) {
    case 1:
        System.out.println("Odd? " + isOdd(number));
        break;

    case 2:
        System.out.println("Power of 2? " + isPowerOfTwo(number));
        break;

    case 3:
        System.out.println("Two's complement: " + twosComplement(number));
        break;

    default:
        System.out.println("Invalid option.");
}

System.out.println();

input.close();
}

public static boolean isOdd(int n) {
    return (n & 1) == 1;
}

public static boolean isPowerOfTwo(int n) {

```

```
        return n > 0 && (n & (n - 1)) == 0;
    }

    public static int twosComplement(int n) {
        return (~n) + 1;
    }
}
```

```
C:\Users\lucas\.jdk\ms-21.0.8\bin\java.exe "-javaagent
Enter a number: 12
```

```
--- Bitwise Operations Menu ---
```

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

```
Choose an option: 1
```

```
The number is even.
```

```
Process finished with exit code 0
```

```
|
```

```
C:\Users\lucas\.jdk\ms-21.0.8\bin\java.exe "-javaagent:C:\Pro
Enter a number: 12
```

```
--- Bitwise Operations Menu ---
```

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

```
Choose an option: 2
```

```
The number is NOT a power of 2.
```

```
Process finished with exit code 0
```

```
C:\Users\lucas\.jdk\ms-21.0.8\bin\java.exe "-javaagent:C
Enter a number: 12
```

```
--- Bitwise Operations Menu ---
```

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

```
Choose an option: 3
```

```
Two's complement: -12
```

```
Process finished with exit code 0
```

Ready? Then save this file and export it as a pdf file with the name: [week2.pdf](#)